# Lab assignment 5

# 1. Preparation Task

### a. Binary values of the segments for display 0 to 9 on a common anode 7-segment display.

Digit	A	В	С	D	E	F	G	DP
0	0	0	0	0	0	0	1	1
1	1	0	0	1	1	1	1	1
2	0	0	1	0	0	1	0	1
3	0	0	0	0	1	1	0	1
4	1	0	0	1	1	0	0	1
5	0	1	0	0	1	0	0	1
6	0	1	0	0	0	0	0	1
7	0	0	0	1	1	1	1	1
8	0	0	0	0	0	0	0	1
9	0	0	0	0	1	0	0	1

#### b. Common cathode vs anode

In the common cathode display (cc), all the cathode connections of the 7-segments are joined together and connected to ground (logic '0') and the individual segments are illuminated by the application of a High (logic '1') signal via a current limiting resister to forward bias the individual Anode terminals. While in the common anodes of the LED segments are connected together to High (logic '1') and the individual segments are illuminated by the application of the logic "0" (LOW) via a current limiting resistor to their Cathodes.

## 2. 7-segment library

### 2.1 Listing of segment.c library

```
* segment.c
 * Created: 10/21/2020 11:22:21
 * Author: masau
/* Includes -----*/
#define F_CPU 16000000 // MCUs CPU frequency
#include <util/delay.h>
#include "gpio.h"
#include "segment.h"
/* Variables -----*/
// Active-low digit 0 to 9
uint8_t segment_value[] = {
      // abcdefgDP
                   // Digit 0
      0b00000011,
      0b10011111, // Digit 0
0b10011111, // Digit 1
0b00100101, // Digit 2
0b00001101, // Digit 3
0b10011001, // Digit 4
      0b01001001, // Digit 5
      0b01000001,
                 // Digit 6
      0b00011111,
                  // Digit 7
      0b00000001,
                  // Digit 8
      0b00001001}; // Digit 9
// Active-high position 0 to 3
uint8 t segment position[] = {
      // p3p2p1p0....
      0b00010000, // Position 0
0b00100000, // Position 1
                   // Position 2
      0b01000000,
                   // Position 3
      0b1000000);
/* Function definitions -----*/
void SEG init(void)
   /* Configuration of SSD signals */
   GPIO_config_output(&DDRD, SEGMENT_LATCH);
   GPIO_config_output(&DDRD, SEGMENT_CLK);
   GPIO_config_output(&DDRB, SEGMENT_DATA);
}
/*-----*/
void SEG_update_shift_regs(uint8_t segments, uint8_t position)
```

```
uint8 t bit number;
   segments = segment value[segments];
                                         // 0, 1, ..., 9
   position = segment_position[position]; // 0, 1, 2, 3
// Pull LATCH, CLK, and DATA low
   GPIO write low(&PORTD, SEGMENT LATCH);
   GPIO write low(&PORTD, SEGMENT CLK);
   GPIO_write_low(&PORTB, SEGMENT_DATA);
// Wait 1 us
  _delay_us(1);
// Loop through the 1st byte (segments)
// a b c d e f g DP (active low values)
for (bit_number = 0; bit_number < 8; bit_number++)</pre>
{
    // Output DATA value (bit 0 of "segments")
          if ((segments & 1) == 0)
                 GPIO write low(&PORTB, SEGMENT DATA);
          }
          else
          {
                 GPIO_write_high(&PORTB, SEGMENT_DATA);
          }
    // Wait 1 us
          _delay_us(1);
    // Pull CLK high
          GPIO_write_high(&PORTD, SEGMENT_CLK);
    // Wait 1 us
          _delay_us(1);
    // Pull CLK low
          GPIO_write_low(&PORTD, SEGMENT_CLK);
    // Shift "segments"
    segments = segments >> 1;
}
// Loop through the 2nd byte (position)
// p3 p2 p1 p0 . . . (active high values)
for (bit_number = 0; bit_number < 8; bit_number++)</pre>
{
    // Output DATA value (bit 0 of "position")
          if ((position % 2) == 0)
          {
                 GPIO write low(&PORTB, SEGMENT DATA);
          }
          else
          {
                 GPIO write high(&PORTB, SEGMENT DATA);
          }
```

{


```
// Wait 1 us
          _delay_us(1);
      // Pull CLK high
          GPIO_write_high(&PORTD, SEGMENT_CLK);
      // Wait 1 us
          _delay_us(1);
     // Pull CLK low
          GPIO_write_low(&PORTD, SEGMENT_CLK);
      // Shift "position"
     position = position >> 1;
  }
   // Pull LATCH high
     GPIO_write_high(&PORTD, SEGMENT_LATCH);
  // Wait 1 us
    _delay_us(1);
}
/*----*/
/* SEG clear */
/*----*/
/* SEG_clk_2us */
```

### 2.2 Listing of decimal counter main.c (00 to 59)

```
#include "segment.h"
                          // Seven-segment display library for AVR-GCC
uint8 t ones = 0;
uint8_t tens = 0;
/* Function definitions -----*/
* Main function where the program execution begins. Display decimal
* counter values on SSD (Seven-segment display) when 16-bit
* Timer/Counter1 overflows.
int main(void)
{
   // Configure SSD signals
   SEG_init();
   // Test of SSD: display number '3' at position 0
   //SEG_update_shift_regs(4, 0);
      /* Configure 8-bit Timer/Counter0
    * Set prescaler and enable overflow interrupt */
      TIMO_overflow_4ms();
      TIMO_overflow_interrupt_enable();
   /* Configure 16-bit Timer/Counter1
    * Set prescaler and enable overflow interrupt */
      TIM1_overflow_262ms();
      TIM1_overflow_interrupt_enable();
   // Enables interrupts by setting the global interrupt mask
      sei();
   // Infinite loop
   while (1)
   {
       /* Empty loop. All subsequent operations are performed exclusively
        * inside interrupt service routines ISRs */
   // Will never reach this
   return 0;
}
/* Interrupt service routines -----*/
* ISR starts when Timer/Counter0 overflows. Display value on SSD.
ISR(TIMER0 OVF vect)
       static uint8_t position = 0;
       if(position == 0)
       {
              SEG_update_shift_regs(ones, 0);
              position = 1;
       }
```

```
else
        {
                SEG_update_shift_regs(tens, 1);
position = 0;
        }
}
/**
* ISR starts when Timer/Counter1 overflows. Increment decimal counter
ISR(TIMER1_OVF_vect)
{
       ones++;
       if(ones > 9)
              ones = 0;
              tens++;
              if(tens > 5)
                      tens = 0;
              }
       }
}
```

## 2.3 7-segment Circuit

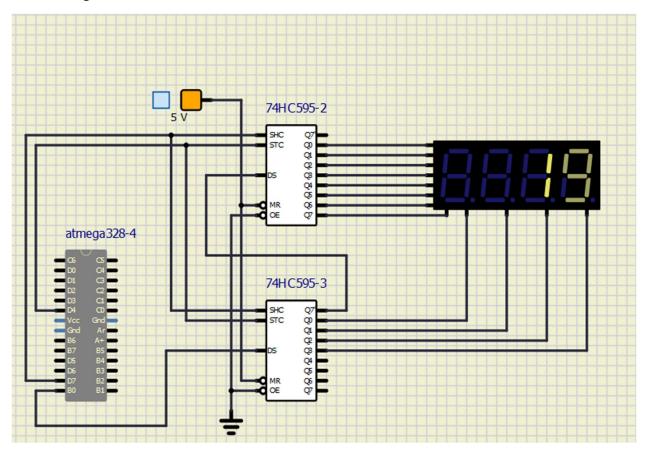

## 3 Snake application

## 1. Snake Look-up table

Segment	Binary code	snake position		
NON	0b11111111			
А	0b01111111	-		
В	0b10111111	I		
С	0b11011111	l		
D	0b11101111	_		
E	0b11110111	l		
F	0b11111011	ı		

#### 2. Main.c

```
* snake.c
* Created: 10/21/2020 11:18:03
* Author : masau
* Decimal counter with 7-segment output.
* ATmega328P (Arduino Uno), 16 MHz, AVR 8-bit Toolchain 3.6.2
* Copyright (c) 2018-2020 Tomas Fryza
* Dept. of Radio Electronics, Brno University of Technology, Czechia
* This work is licensed under the terms of the MIT license.
/* Includes -----*/
#include "timer.h" // Timer library for AVR-GCC
#include "segment.h"
               // Seven-segment display library for AVR-GCC
uint8_t ones = 0; // first digit on the 4-digit 7-segment display
uint8_t tens = 0; // second digit on the display
/* Function definitions -----*/
```

```
/**
* Main function where the program execution begins. Display decimal
 * counter values on SSD (Seven-segment display) when 16-bit
* Timer/Counter1 overflows.
int main(void)
{
   // Configure SSD signals
   SEG_init();
   // Test of SSD: display number '3' at position 0
   //SEG update shift regs(4, 0);
      /* Configure 8-bit Timer/Counter0
    * Set prescaler and enable overflow interrupt */
      TIMO_overflow_1ms();
      TIMO overflow interrupt enable();
   /* Configure 16-bit Timer/Counter1
    * Set prescaler and enable overflow interrupt */
      TIM1_overflow_262ms();
      TIM1_overflow_interrupt_enable();
   // Enables interrupts by setting the global interrupt mask
      sei();
   // Infinite loop
   while (1)
   {
       /* Empty loop. All subsequent operations are performed exclusively
        * inside interrupt service routines ISRs */
   }
   // Will never reach this
   return 0;
}
/* Interrupt service routines -----*/
 * ISR starts when Timer/Counter0 overflows. Display value on SSD.
ISR(TIMER0_OVF_vect)
 {
       static uint8_t position = 0;
       if(position == 0)
              SEG update shift regs(ones, 0);
              position = 1;
       }
       else
       {
              SEG_update_shift_regs(tens, 1);
              position = 0;
       }
}
```

```
* ISR starts when Timer/Counter1 overflows. Increment decimal counter
ISR(TIMER1_OVF_vect)
{
       if(tens == 0)
              ones++;
              if(ones > 4)
                     ones = 0;
                     tens = 4;
              }
       }
       else if (tens > 3)
              tens++;
              if (tens > 6)
                    tens = 1;
      }
else if (tens == 1)
              tens = 0;
              ones = 1;
       }
}
```